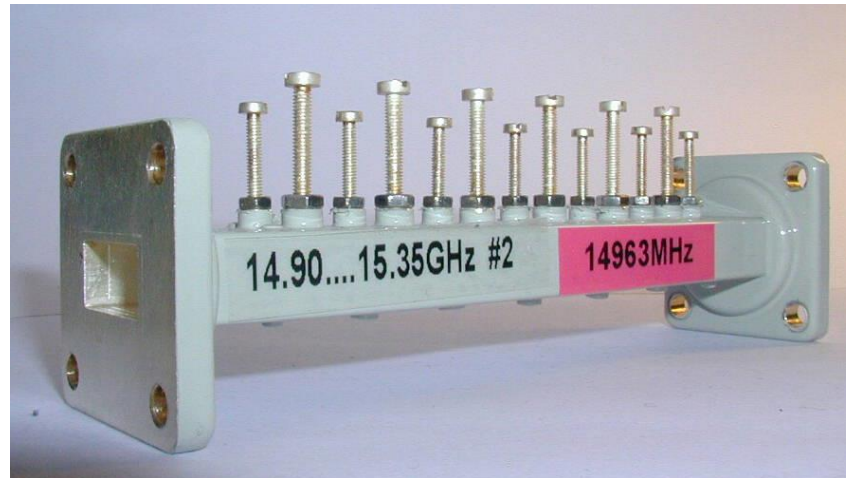


Step-by-step procedure for design of waveguide filters with HFSS



Kjetil Folgerø

Nera Telecommunications, Norway

kfo@nera.no

Outline

- Filters at Nera
- Introduction / Motivation
- Step-by-step design procedure
- Detailed design example
- Other examples
- Conclusion



Filters at Nera

- Channel filters:
 - Narrow-band ($< 1\%$) \Rightarrow tuning
 - 2 GHz - 15 GHz
- Sub-band filters:
 - "Broad-band" (2-5%) \Rightarrow no tuning
 - 15 GHz - 40 GHz


- Waveguide (inductive iris, circular posts)
- Dielectric resonator

- Other waveguide components
 - OMT, bends, hybrids, transitions, ...


Motivation

- There exist many EM computer programs for design of waveguide filters, but these are limited to specific filter topologies or coupling structures
 - ⇒ need for a general tool like HFSS
- HFSS can be used for global optimization of filters, but optimization is slow for large structures with a large number of optimization variables
 - ⇒ need for a better design procedure
- Solution:
 - Apply well known circuit theory synthesis methods in combination with HFSS

Global optimization

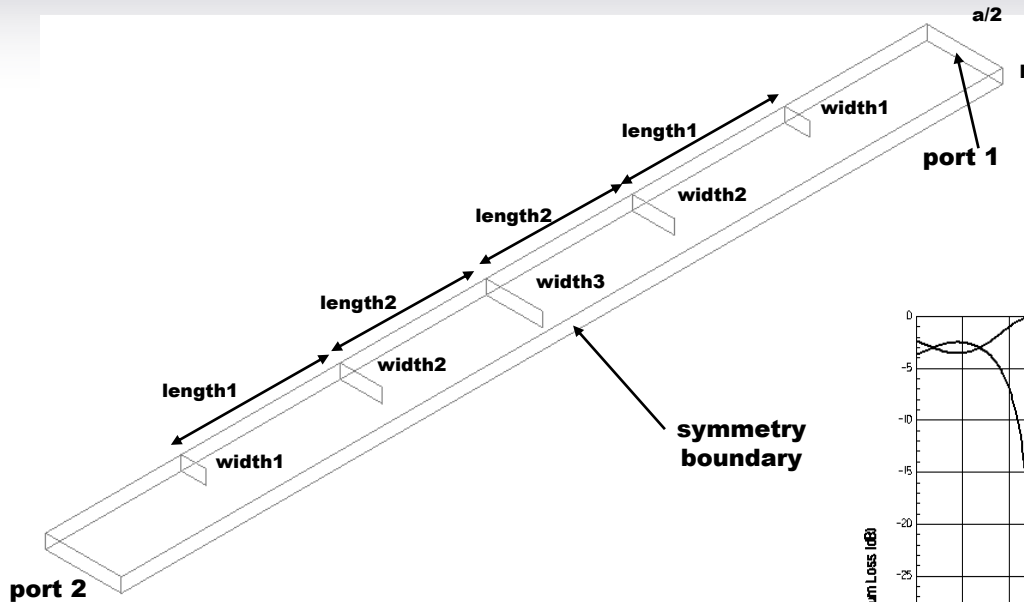

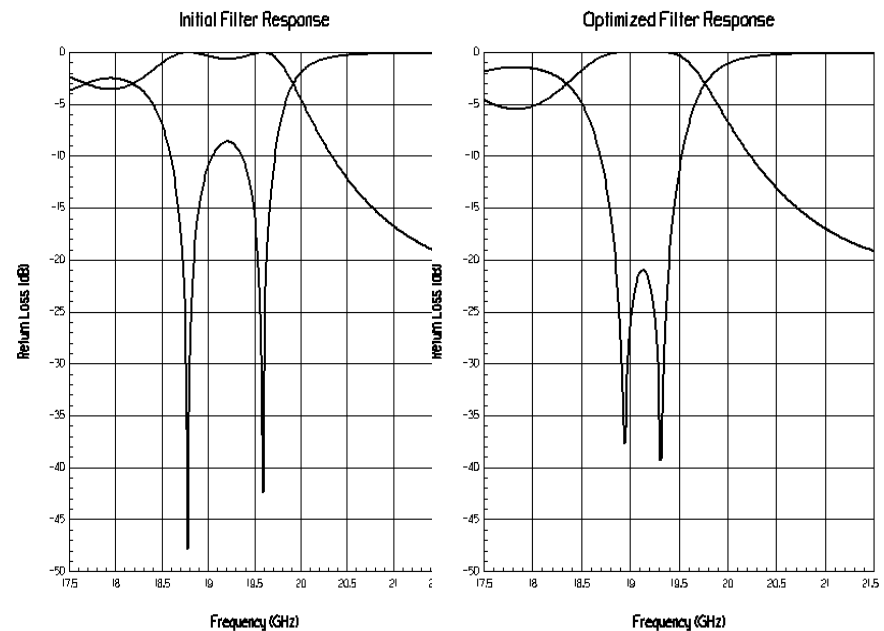
- many variables to optimize,
- long simulation time,
- non-optimum solution



Brian Gray, Ansoft, "External Optimization Using Ansoft HFSS", AB053-9905, May 1999.

Michael Brenneman, Ansoft, "Ansoft HFSS V7: Optimetrics™ Case Studies of Optimization and Parametrics", 1999 HFSS User Workshop

Equivalent circuit

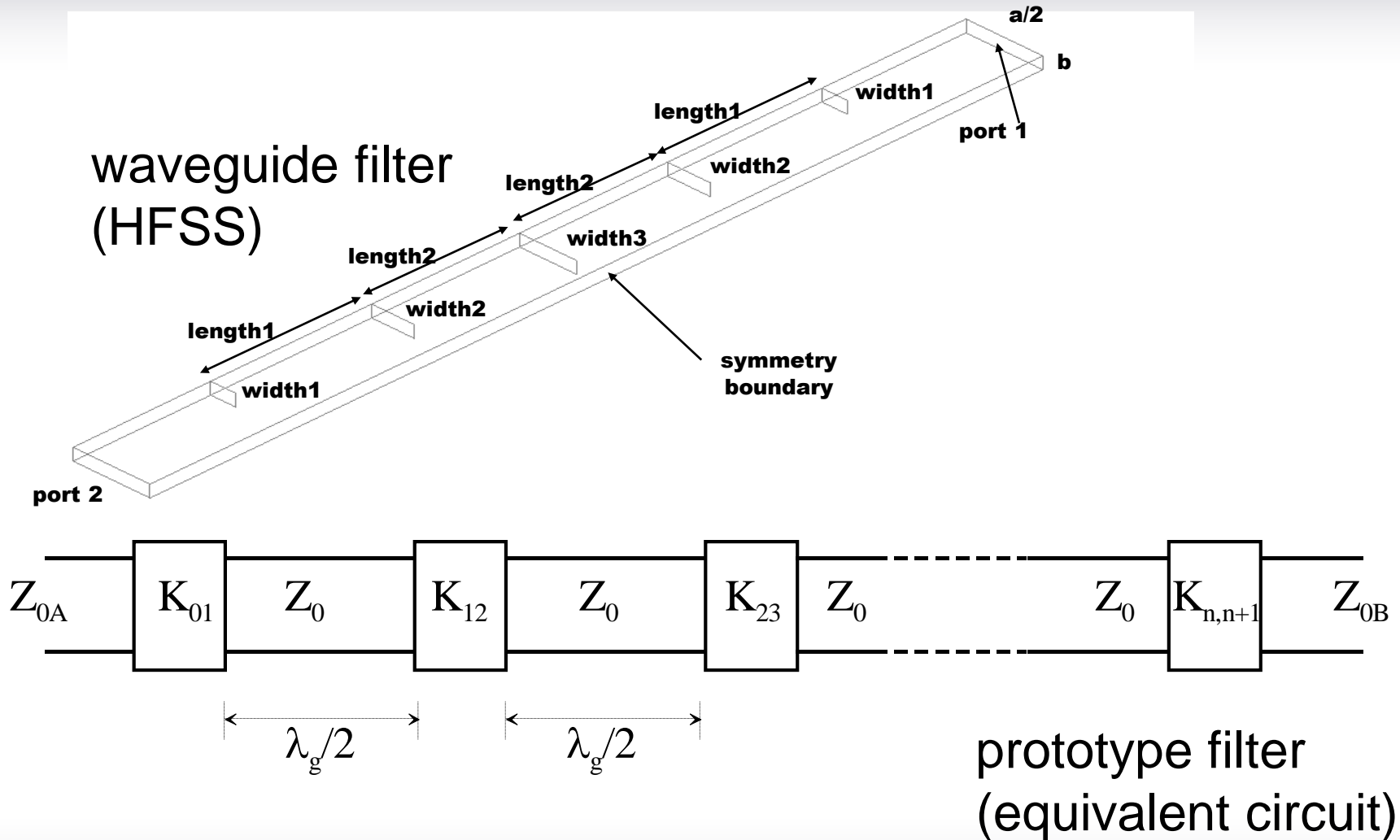


S B Cohn "Direct-coupled-resonator filters" Proc. IRE pp187-96, Feb 1957


Step-by-step procedure

- optimization of one dimension in each step

waveguide filter
(HFSS)

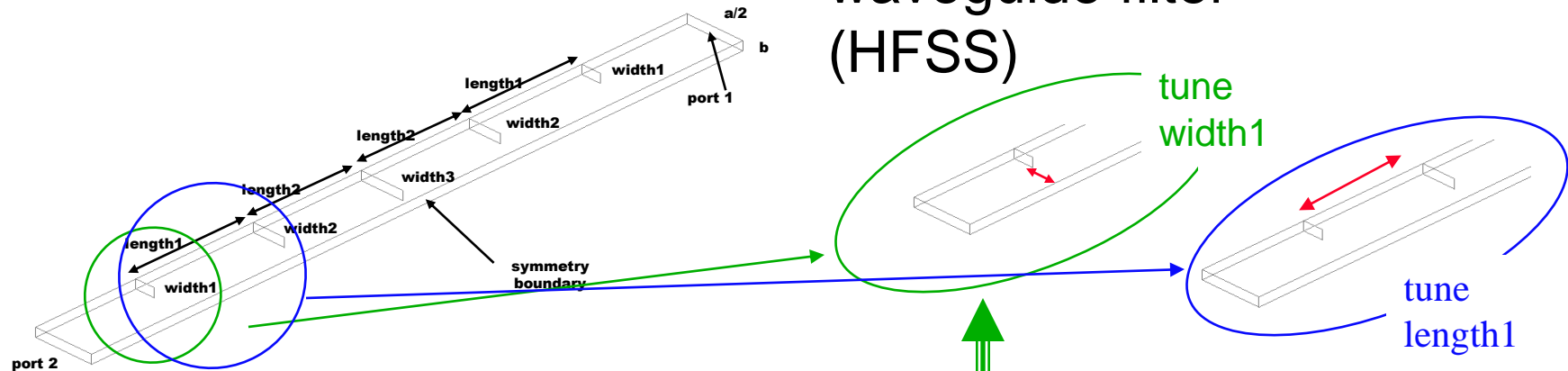

optimize / tune

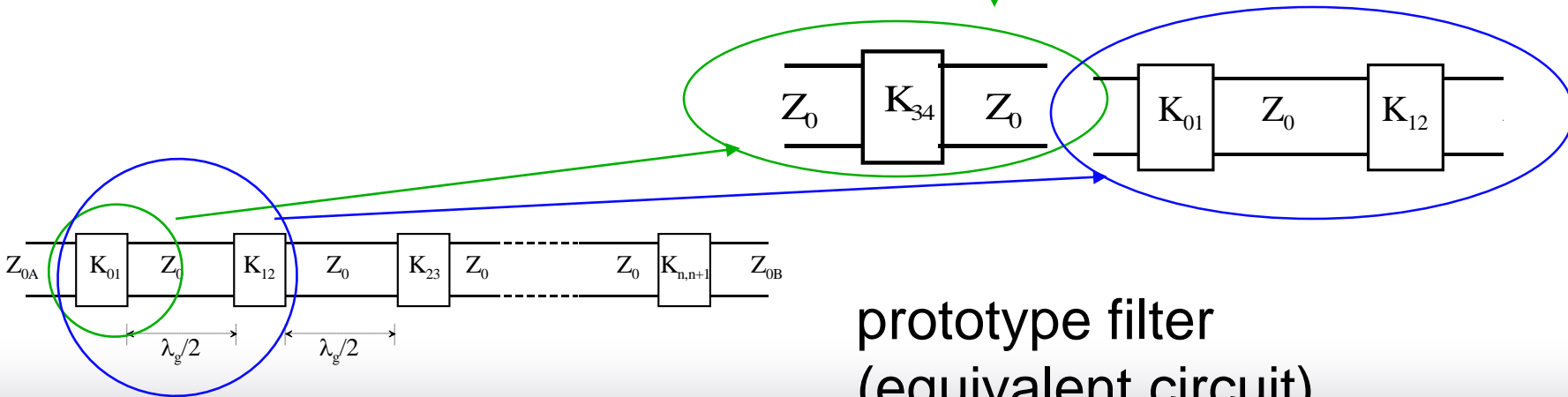

prototype filter
(equivalent circuit)

Step-by-step procedure

Advantages:

- Simulation of small structures in each step => fast simulation
- Only one dimension is optimized in each step => fast convergence


Procedure:

- 1) Obtain prototype filter from filter specifications
- 2) For all couplings: Optimize coupling with HFSS to give the right K-inverter value at the center frequency
- 3) For all resonators: Calculate resonator length, fine tune parameter with HFSS

Design Example

Filter with inductive posts


WR62

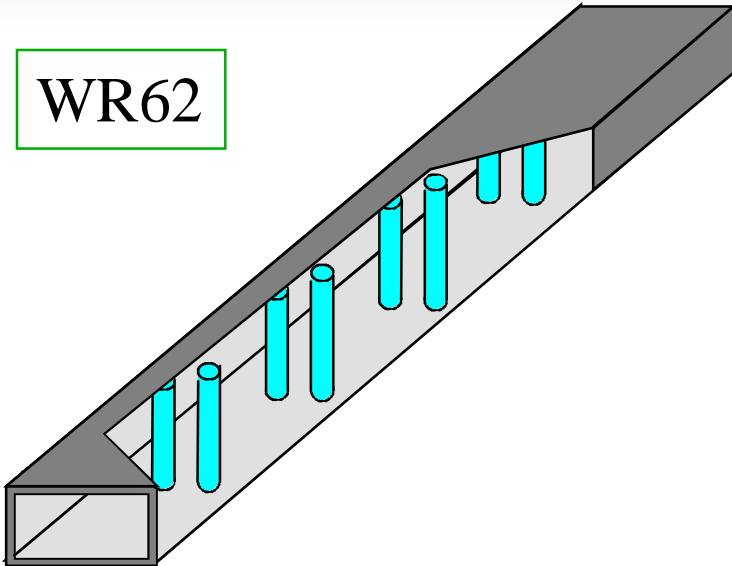

Design Requirements

- $f_0 = 15.35$ GHz BW= 32 MHz
- $S_{11} < -20$ dB
- $S_{21} < -40$ dB @ $f_0 \pm 40$ MHz


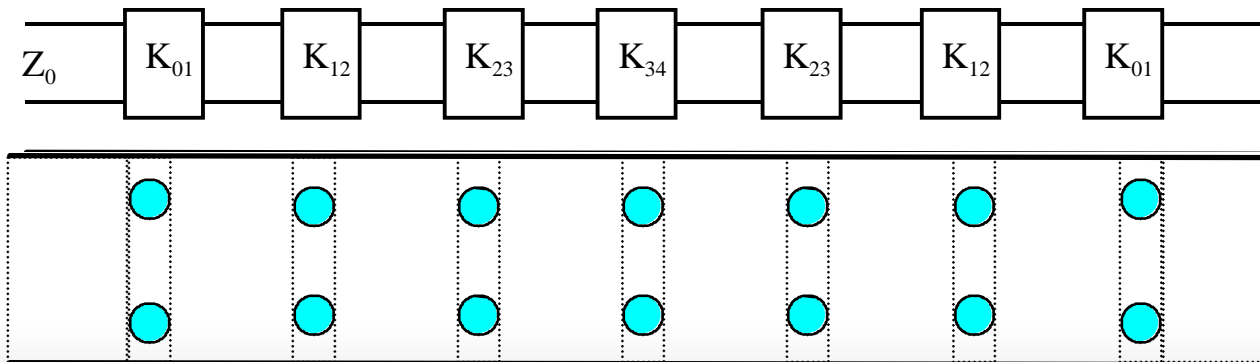
The filter shall be tunable from 14.9 to 15.35 GHz



Step-by-step procedure


step 1: Prototype filter

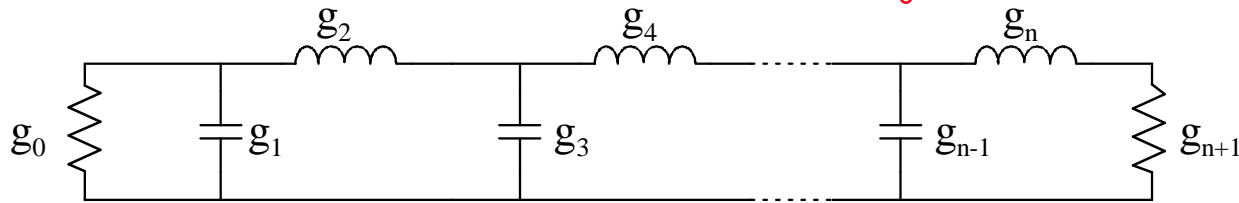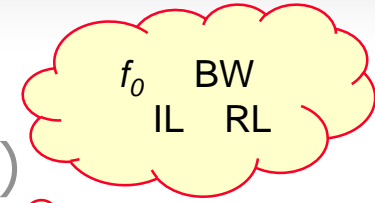1a) Obtain low-pass prototype parameters (g_i) from filter specifications (see e.g. Matthaei*)



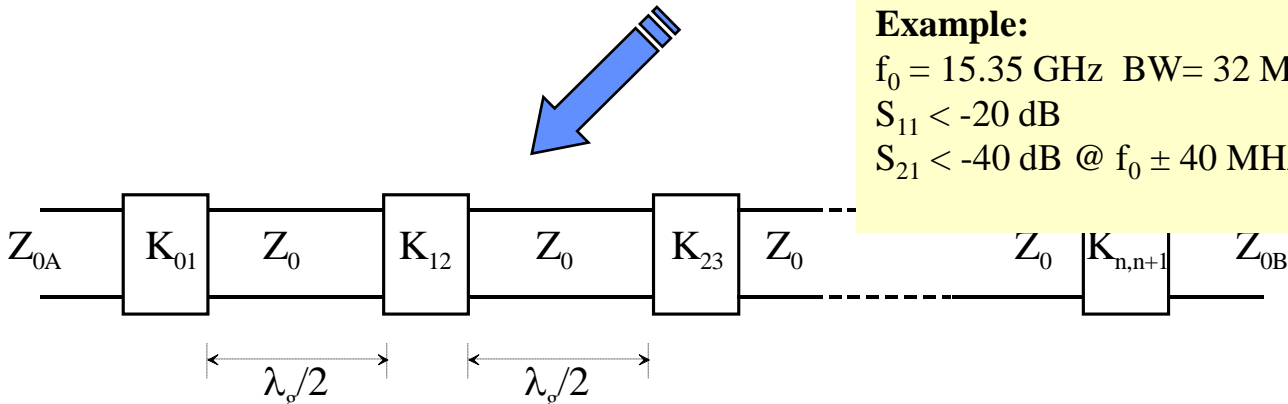Example:
 $f_0 = 15.35$ GHz BW= 32 MHz
 $S_{11} < -20$ dB
 $S_{21} < -40$ dB @ $f_0 \pm 40$ MHz

- 6th order Chebychev filter**
prototype elements
- $g_0 = 1.0000$
 - $g_1 = 0.8836$
 - $g_2 = 1.3966$
 - $g_3 = 1.7894$
 - $g_4 = 1.5528$
 - $g_5 = 1.6095$
 - $g_6 = 0.7667$
 - $g_7 = 1.1524$




*Matthaei, Young and Jones "Microwave filters, impedance-matching networks, and coupling structures", Artech House, Norwood, MA, 1992

Step-by-step procedure

step 1: Prototype filter

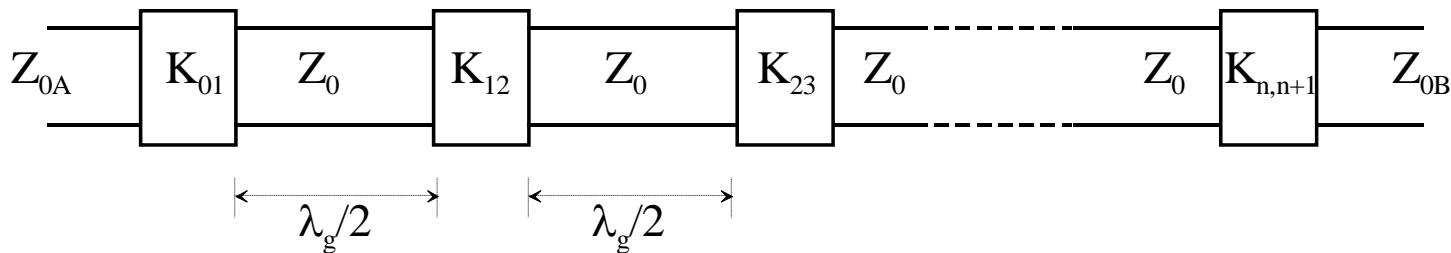1b) Calculate K-inverters (band-pass prototype parameters)



$$K'_{01} = \frac{K_{01}}{Z_{0A}} = \sqrt{\frac{\pi}{2} \frac{W_{\lambda A}}{g_0 g_1}}$$

$$K'_{i,i+1} = \frac{K_{i,i+1}}{\sqrt{Z_{0i} Z_{0,i+1}}} = \frac{\pi W_{\lambda i}}{2} \sqrt{\frac{1}{g_i g_{i+1}}}$$

$$K'_{n,n+1} = \frac{K_{n,n+1}}{Z_{0B}} = \sqrt{\frac{\pi}{2} \frac{W_{\lambda B}}{g_n g_{n+1}}}$$

$$W_{\lambda i} = \left(\frac{\lambda_{gi0}}{\lambda_0} \right)^2 \frac{\Delta f}{f_0}$$


Example:

$$\begin{aligned} K'_{01} &= 0.0775 \\ K'_{12} &= 0.0048 \\ K'_{23} &= 0.0034 \\ K'_{34} &= 0.0032 \end{aligned}$$


Step-by-step procedure

step 2: Optimize couplings

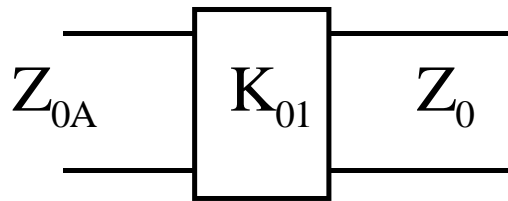- For all couplings: Optimize coupling to give the right K-inverter value at the center frequency



$$S_{21} = \frac{2}{jK' + j/K'}$$

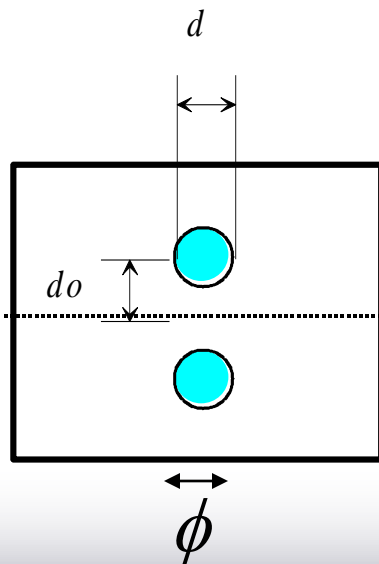

Coupling S_{21} (dB)

1	-16.14
2	-40.40
3	-43.47
4	-43.93
5	-43.47
6	-40.40
7	-16.14



diameter

$d_1 = 2.50$ mm
$d_2 = 3.50$ mm
$d_3 = 3.50$ mm
$d_4 = 3.50$ mm
$d_5 = 3.50$ mm
$d_6 = 3.50$ mm
$d_7 = 2.50$ mm



offset

$do_1 = 3.845$ mm
$do_2 = 3.135$ mm
$do_3 = 2.960$ mm
$do_4 = 2.972$ mm
$do_5 = 2.960$ mm
$do_6 = 3.135$ mm
$do_7 = 3.845$ mm

Step-by-step procedure

step 3: Optimize resonator lengths

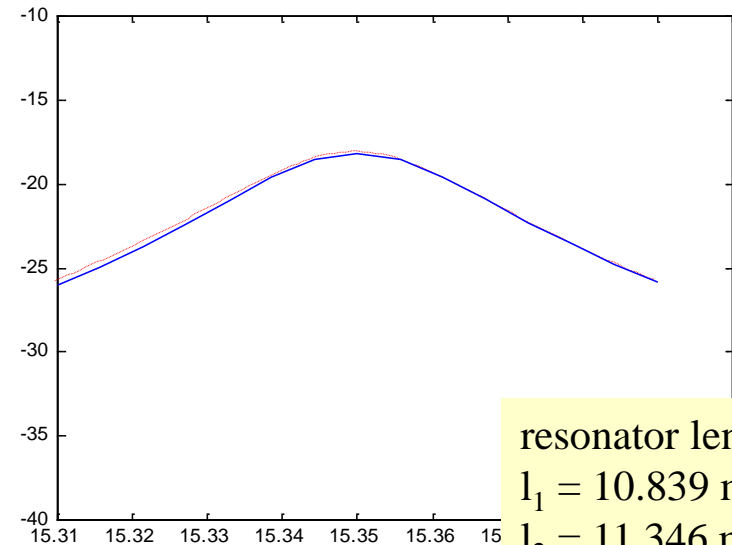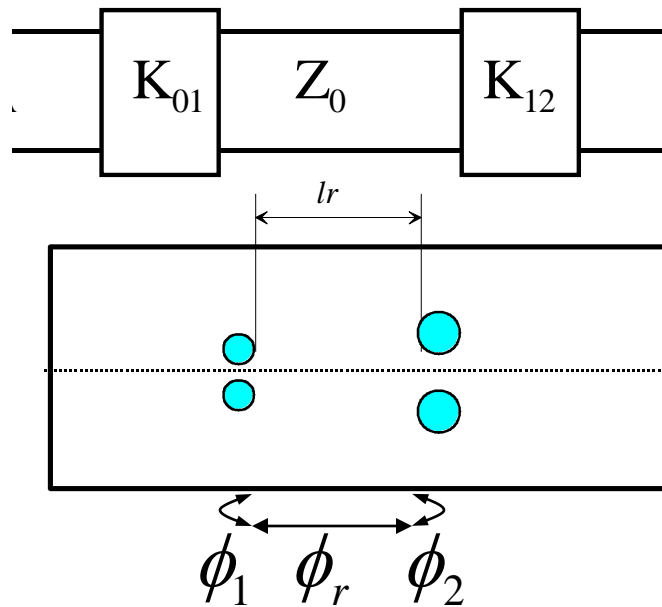- For all resonators: calculate resonator length, fine tune until the structure resonates at the center frequency



resonator length
 $l_1 = 10.839$ mm
 $l_2 = 11.346$ mm
 $l_3 = 11.395$ mm
 $l_4 = 11.395$ mm
 $l_5 = 11.346$ mm
 $l_6 = 10.839$ mm



$$\phi_r = \pi - \frac{1}{2}(\phi_1 + \phi_2)$$

$$l = \frac{\phi_r \lambda_g}{2\pi}$$

Measurements

Filter with inductive posts

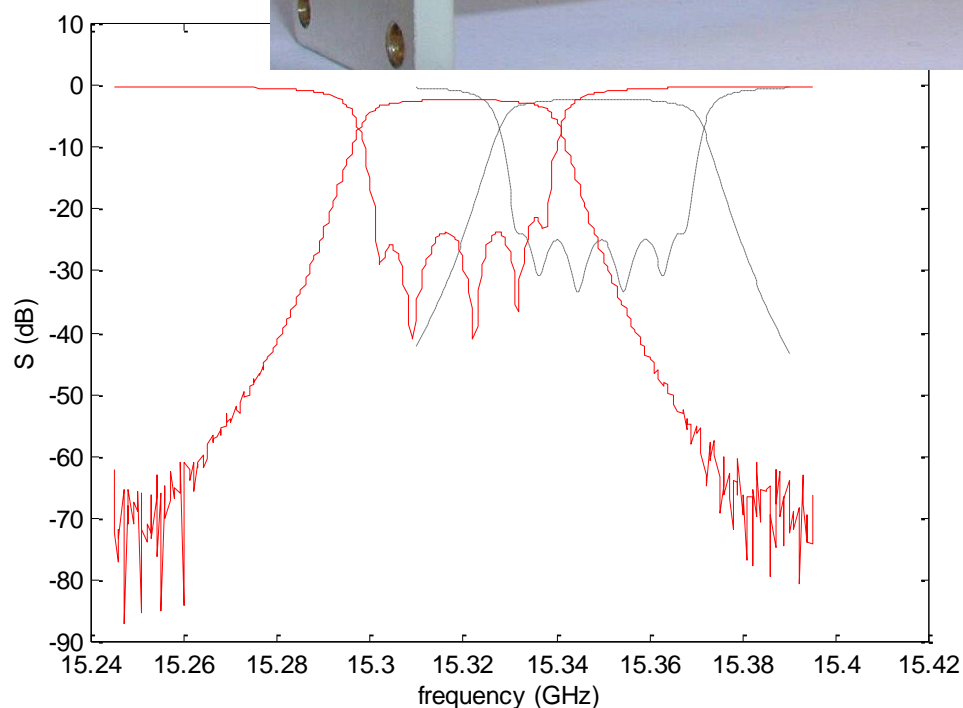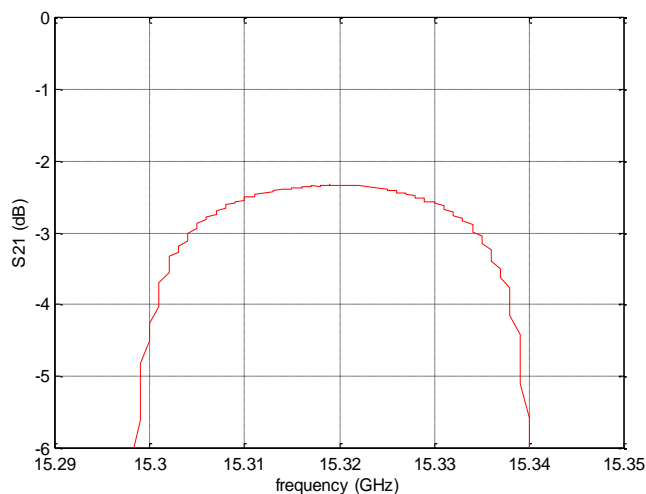
- Designed at 15.35 GHz
- Tunable from 14.9 to 15.35 GHz
- Measured at 15.32 GHz



Measurements

Filter with inductive posts


- data centered on f_0

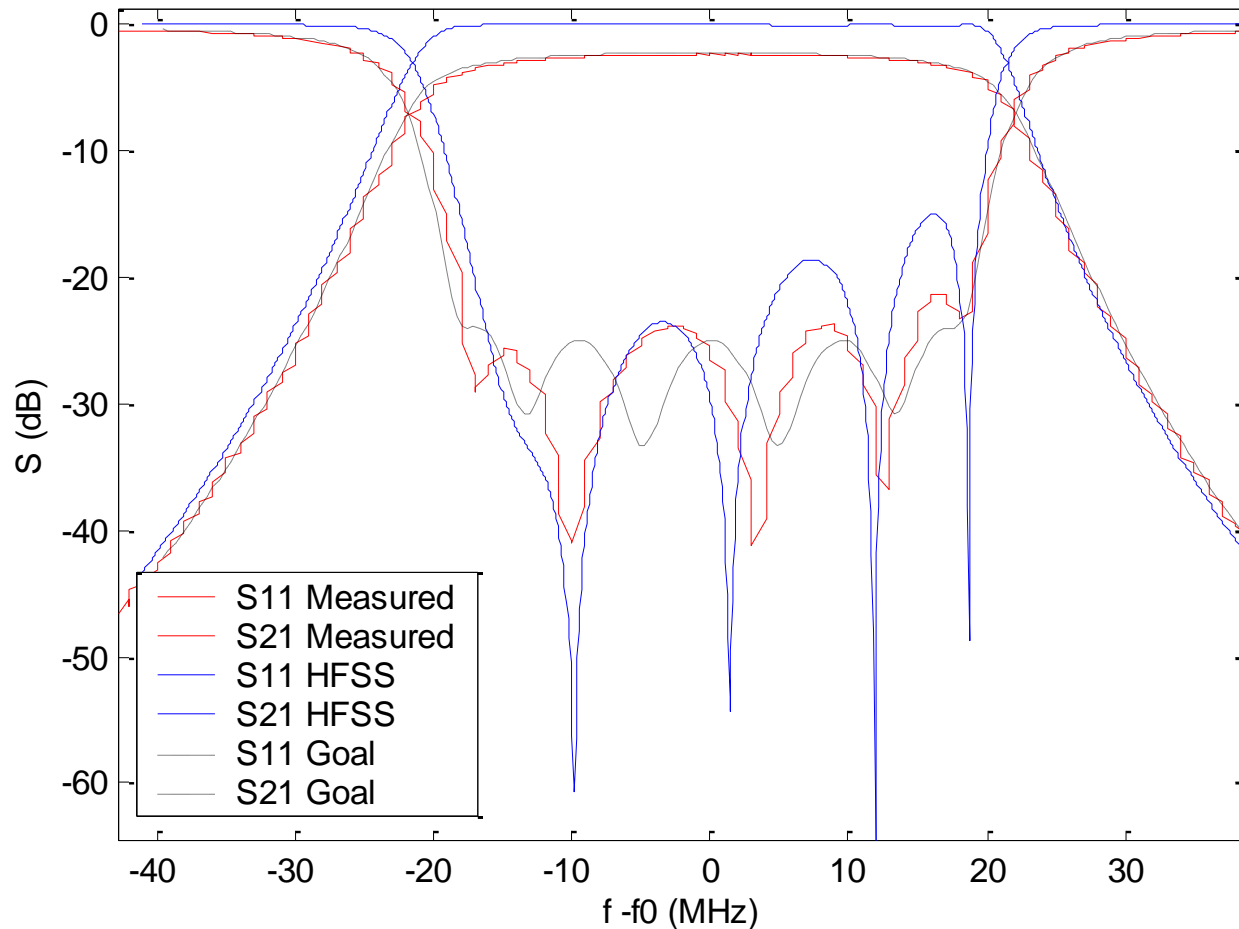

Simulation Setup

Filter with inductive posts

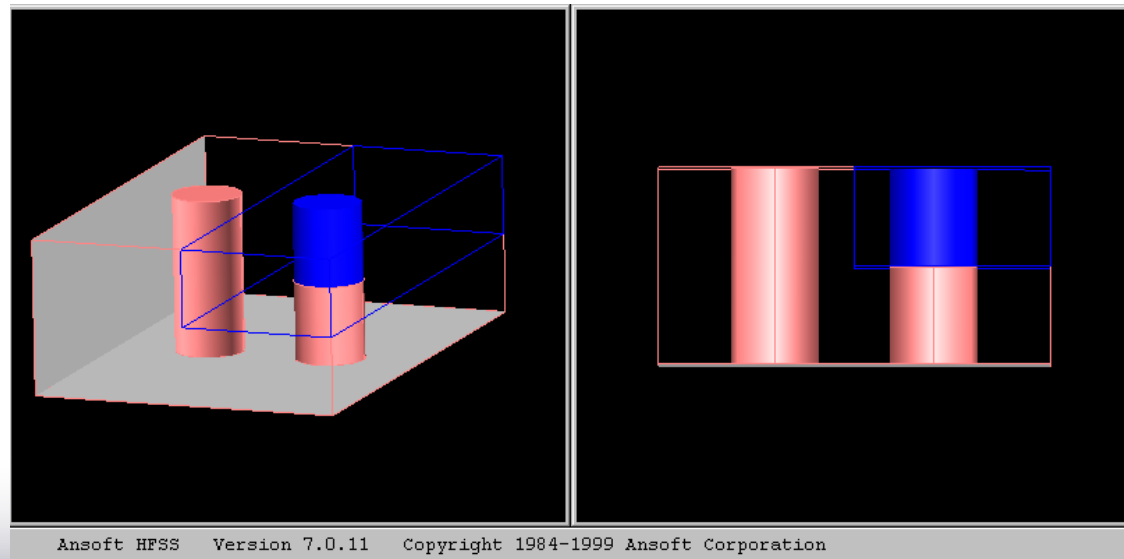- The procedure is automated with Octave (/Matlab)
- Assume infinite conductivity
- 3 frequency points enough to determine the resonator length
- Use symmetry (E- and H-plane)



Simulation Data



Filter with inductive posts

- Couplings:
 - 10 adaptive passes
 - 2274 tetrahedra
 - appr. 1 min solution time per simulation
- Resonators
 - 10 adaptive passes
 - 3871 tetrahedra
 - appr. 2 min solution time per simulation


Dual Pentium III 866 MHz, 768 MB RAM

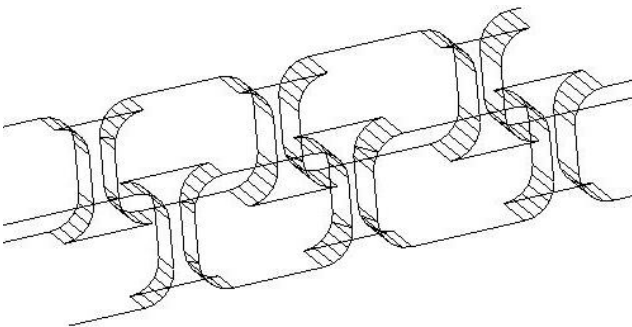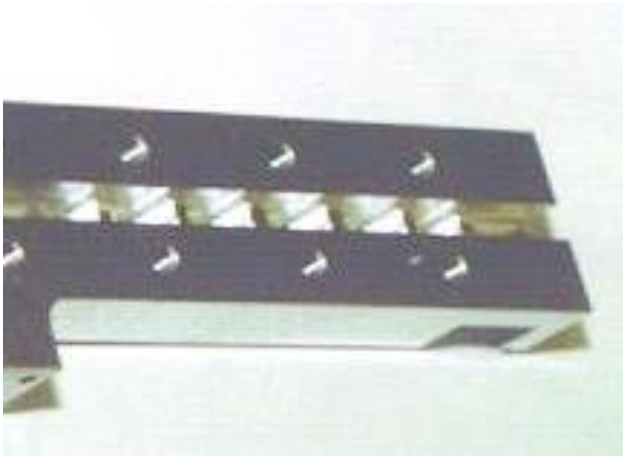Example

Inductive iris filter with "rounded" corners



S11 [dB], S21 [dB]

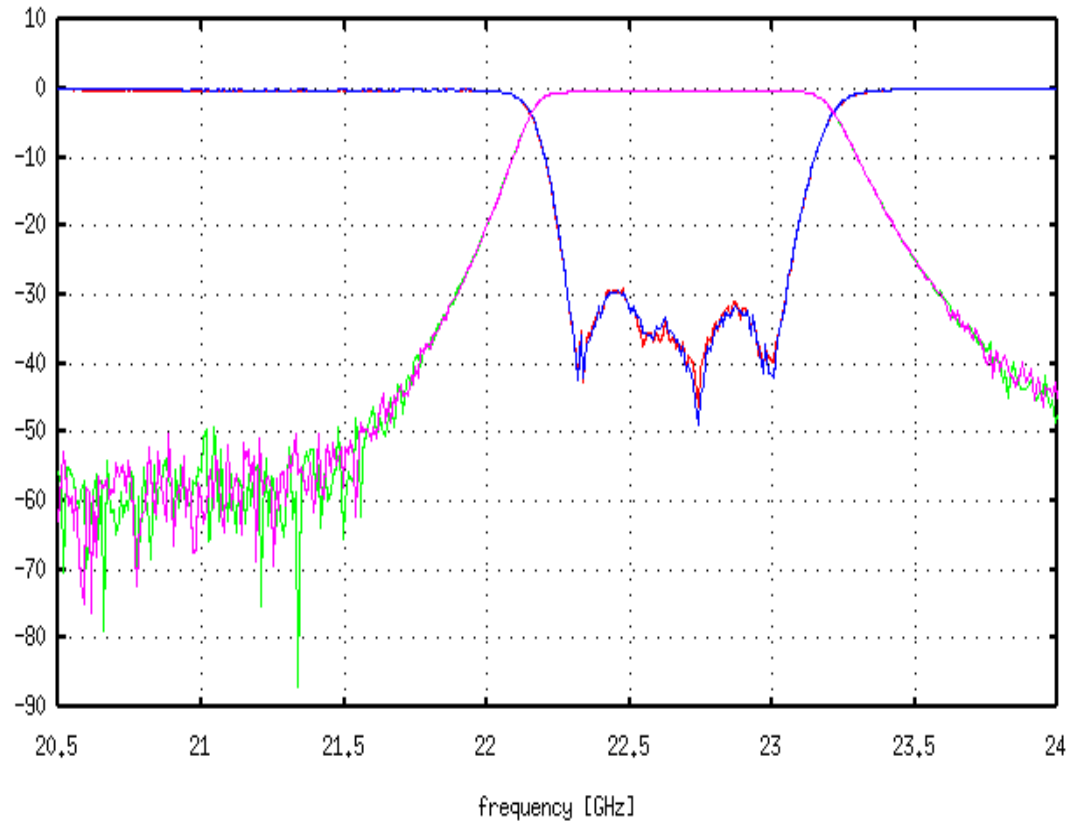

23GHzr2B1d3, s2p, S11



23GHzr2B1d3, s2p, S21

23GHzr2B2d3, s2p, S11

23GHzr2B2d3, s2p, S21

Example

Folded inductive iris filter

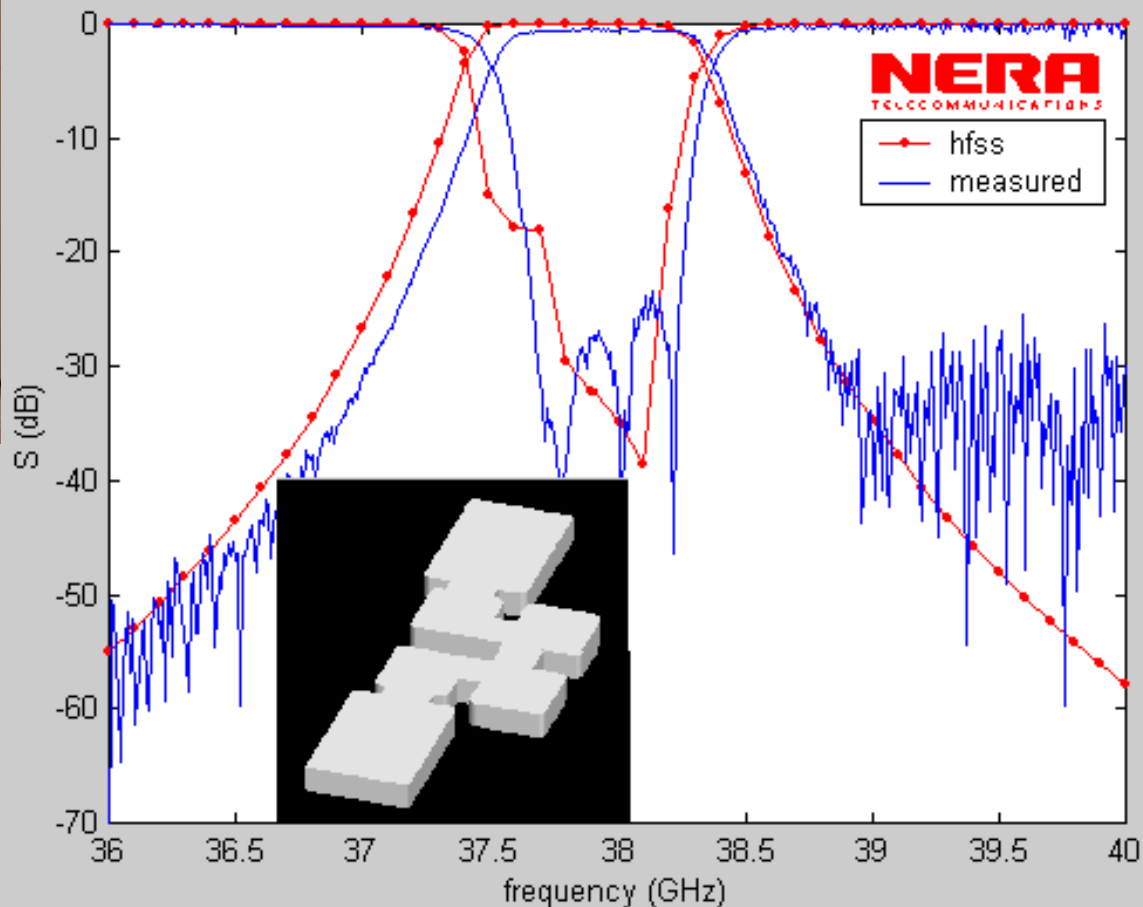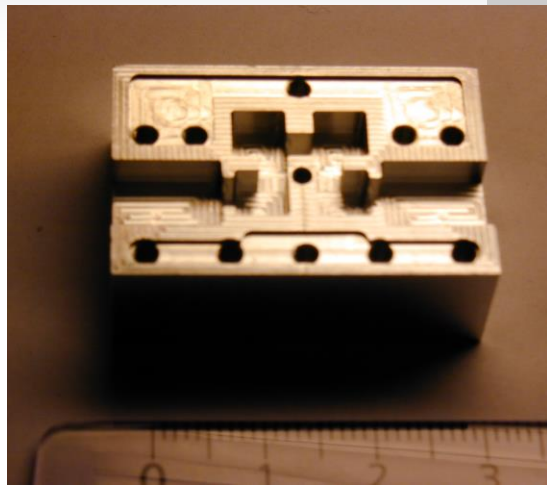


Design procedure:

M. Guglielmi, *Simple CAD procedure for microwave filters and multiplexers*, IEEE Trans. Microwave Theory Tech., vol 42, pp 1347-1352, July 1994

Example



Power divider

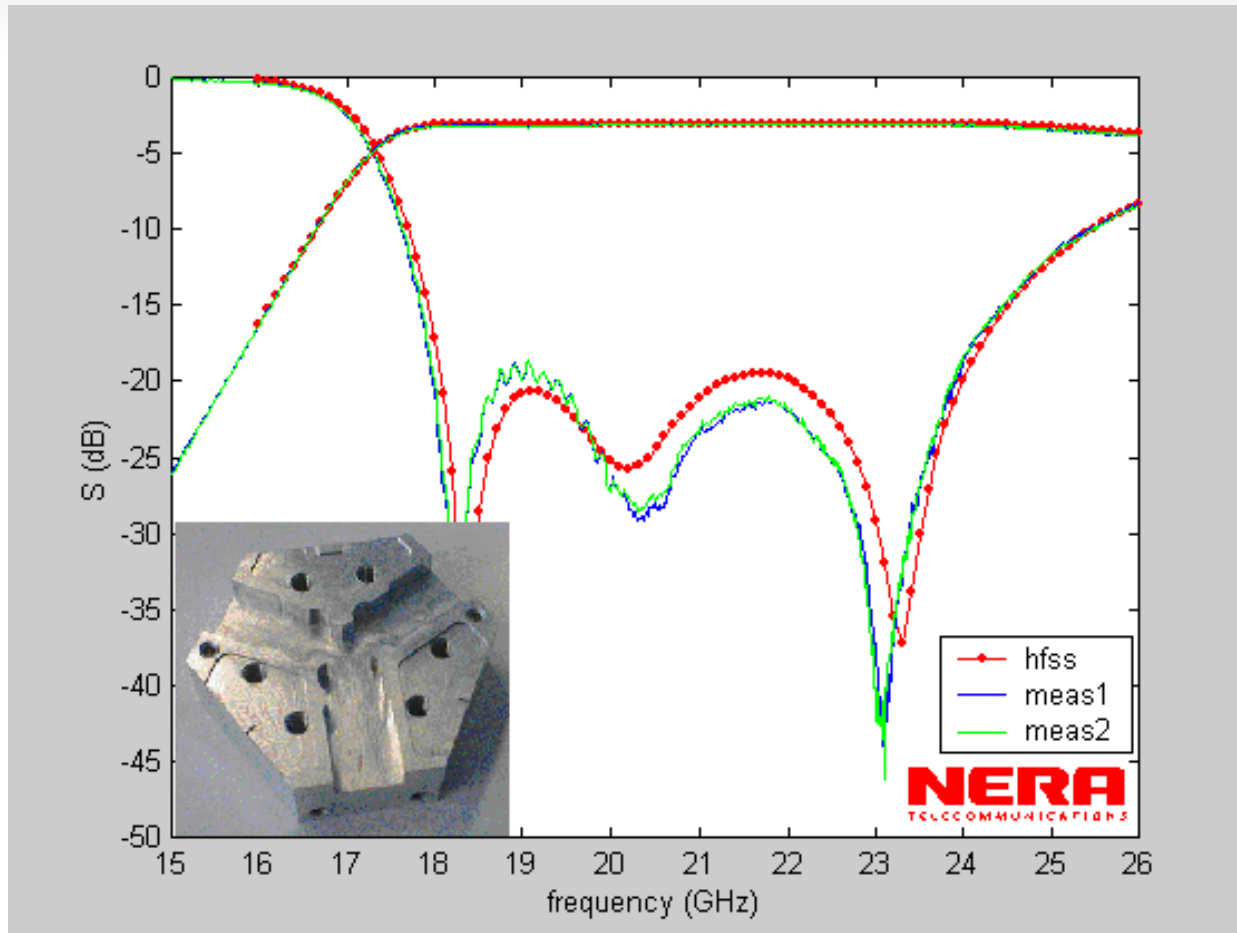

M Guglielmi, B Ginemo, T Kjode "A new equiripple power splitter for radio link applications", Proc. 28th European Microwave Conf ,vol 2, pp 30, 1998

Refinements of the design-procedure

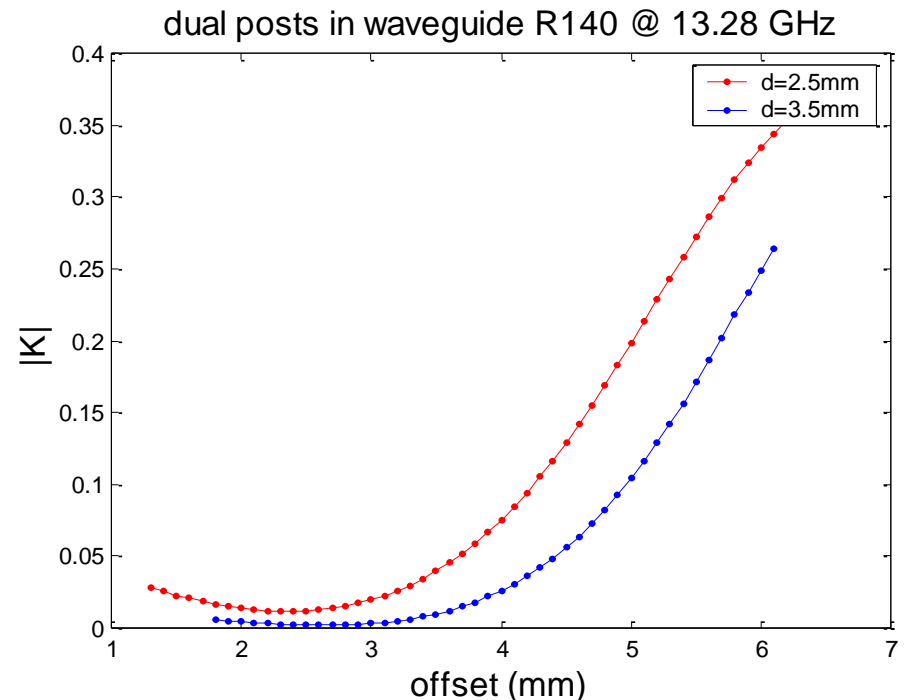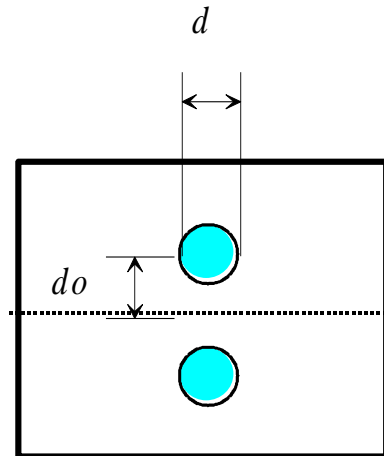- Consider other prototype filters for broadband filters
 - see e.g. S Yin, T. Vasilyeva, P Pramanick “Use of three-dimensional field simulators in the synthesis of waveguide round rod bandpass filters”, Int J RF and Microwave CAE, vol 8, no 6, pp 484-497, 1998
- Build coupling databases



Conclusion

- Easy-to-use design procedure
- Fast convergence of the optimizations because only one parameter is optimized in each step
- Fast solution times because all simulated structures are small
- This design procedure allows us to use HFSS for controlled design of filters - not only for design verification and fine tuning